

Name: Siddhartha Dhar

VHDL Program for 4 bit Asynchronous Up/Down Counter with PreSet and Clear

Git-hub: Siddhartha1999

Problem Statement:


VHDL Structural code for 4 bit Up Down Asynchronous Counter with Asynchronous SET and CLR

Environment Used : Xilinx 14.7 ISE Design Suite

Design of Circuit Diagram :

Let make the Design using 4 JK Flip Flops

 Properties of the JK Flip Flop that had been made as an Component in the Counter Circuit




(J = 0) and (K = 0) then --- No Change
(J = 0) and (K = 1) then --- RESET
(J = 1) and (K = 0) then --- SET
(J = 1) and (K = 1) then --- Toogle

(SET = 1) then Set the Counter Irrespective of Clock
(CLR = 1) then Clear the Counter Irrespective of Clock

The JK Flip Flop is Edge Triggered


Control Block Component

 

If the Control = '1' then Q will propagated to Y
else Q' will be propagated to Y

Control => UP'/DOWN (i.e. when Control is 0 then Count UP else Count Down)

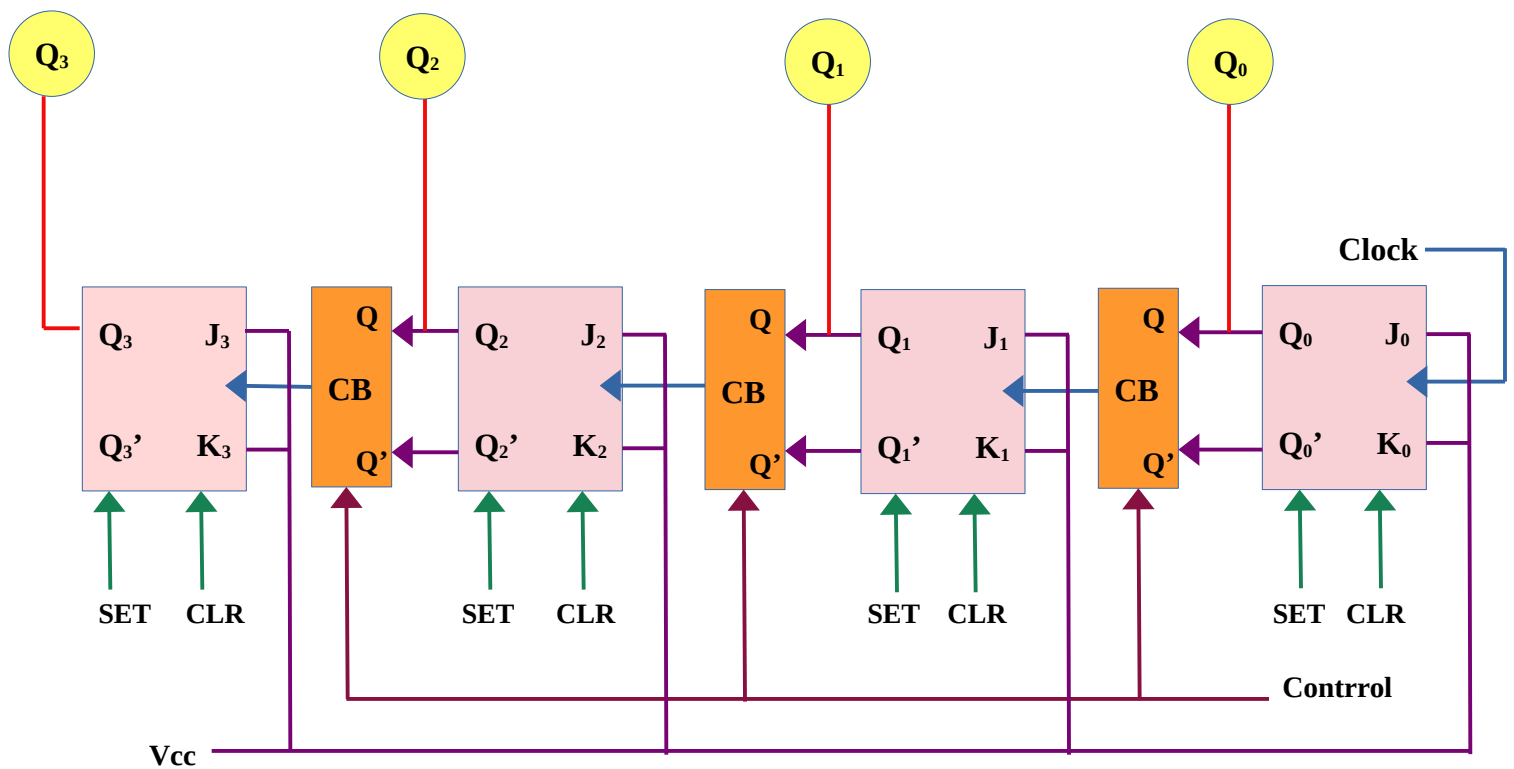Now let us have a look at the Asynchronous Design of the 4 bit up-down counter with Preset and Clear



VHDL Code Implementing 4 bit Asynchronous Up Down Counter using Structural Modeling :

```
-----
-- University:      University of Calcutta
-- Engineer:        Siddhartha Dhar
--
-- Module Name:     Counter_UD - Behavioral
-----

library IEEE;
use IEEE.STD_LOGIC_1164.ALL;

entity Counter_UD is
    Port ( CLOCK : in  STD_LOGIC; -- System Clock
          SET : in  STD_LOGIC;    -- Asynchronous Preset
          CLR : in  STD_LOGIC;    -- Asynchronous Clear
          CONTROL : in  STD_LOGIC; -- Control is ( UP'/DOWN )
          Q : out  STD_LOGIC_VECTOR (3 downto 0);
          Qb : out  STD_LOGIC_VECTOR (3 downto 0));
end Counter_UD;

architecture COUNTER_UD_ARCH of Counter_UD is
    -----JK Flip Flop component
    component JK_FF
        Port ( CLOCK : in  STD_LOGIC;
              J : in  STD_LOGIC;
              K : in  STD_LOGIC;
              SET : in  STD_LOGIC;
              CLR : in  STD_LOGIC;
              Q : out  STD_LOGIC;
              Qb : out  STD_LOGIC);
    end component;

    -----Control Block Component to select the
    counting order (UP/DOWN)
    component Control_Block
        Port ( Control : in  STD_LOGIC;
              Q : in  STD_LOGIC;
              Qb : in  STD_LOGIC;
              Y : out  STD_LOGIC);
    end component;

    -----Signal Definitions
    signal F: STD_LOGIC_VECTOR(3 downto 0);
    signal C: STD_LOGIC_VECTOR(3 downto 0);
    signal CLK: STD_LOGIC_VECTOR(2 downto 0);
```

```

begin

T0: JK_FF PORT MAP(CLOCK=>CLOCK, J=>'1', K=>'1', SET=>SET, CLR=>CLR, Q=>F(0),
    Qb=>C(0)); -- Q0(JK Flip Flop for the LSB of the Counter)
T1: Control_Block PORT MAP(Control=>Control, Q=>F(0), Qb=>C(0), Y=>CLK(0)); --
    Control Block Q0

T2: JK_FF PORT MAP(CLOCK=>CLK(0), J=>'1', K=>'1', SET=>SET, CLR=>CLR, Q=>F(1),
    Qb=>C(1)); -- Q1(JK Flip Flop)
T3: Control_Block PORT MAP(Control=>Control, Q=>F(1), Qb=>C(1), Y=>CLK(1)); --
    Control Block Q1

T4: JK_FF PORT MAP(CLOCK=>CLK(1), J=>'1', K=>'1', SET=>SET, CLR=>CLR, Q=>F(2),
    Qb=>C(2)); -- Q2(JK Flip Flop)
T5: Control_Block PORT MAP(Control=>Control, Q=>F(2), Qb=>C(2), Y=>CLK(2)); --
    Control Block Q2

T6: JK_FF PORT MAP(CLOCK=>CLK(2), J=>'1', K=>'1', SET=>SET, CLR=>CLR, Q=>F(3),
    Qb=>C(3)); -- Q3(JK FlipFlop for the MSB of the Counter)

Q <= F; -- Sorting the Signal element to the Actual Qouput Q
Qb <= C;
end COUNTER_UD_ARCH;

```

VHDL JK Flip Flop Component Behavioral Modeling :

```
-----
-- University:      University of Calcutta
-- Engineer:        Siddhartha Dhar
--
-----

library IEEE;
use IEEE.STD_LOGIC_1164.ALL;

-----Entity Definition
entity JK_FF is
    Port ( CLOCK : in STD_LOGIC;
           J      : in STD_LOGIC;
           K      : in STD_LOGIC;
           SET    : in STD_LOGIC;
           CLR    : in STD_LOGIC;
           Q      : out STD_LOGIC := '0';
           Qb     : out STD_LOGIC := '1');
end JK_FF;

-----Architecture Definition
architecture JK_FF_ARCH of JK_FF is
begin
    p1: process(CLOCK, SET, CLR)
        variable tmp: STD_LOGIC := '0';
    begin
        if(SET='1')then
            tmp := '1';
            Q <= '1';
            Qb <= '0';
        elsif(CLR='1')then
            tmp := '0';
            Q <= '0';
            Qb <= '1';
        elsif(rising_edge(CLOCK))then --If Clock's Poisitive Edge Trigerred
            if(J='0' and K='0')then    -- No Change
                tmp := tmp;
            elsif(J='1' and K='1')then -- Toogle
                tmp := not tmp;
            elsif(J='0' and K='1')then -- Reset
                tmp := '0';
            else                        -- Set
                tmp := '1';
            end if;
        end if;
        Q <= tmp;
        Qb <= not tmp;
    end process p1;
end JK_FF_ARCH;
```

VHDL Control-Block Component Data Flow Modeling :

```
-----
-- University:      University of Calcutta
-- Engineer:        Siddhartha Dhar
--
-- Module Name:     Control_Block - Behavioral
-----

library IEEE;
use IEEE.STD_LOGIC_1164.ALL;

-----Entity Definition
entity Control_Block is
    Port ( Control : in  STD_LOGIC;
          Q : in  STD_LOGIC;
          Qb : in  STD_LOGIC;
          Y : out  STD_LOGIC);
end Control_Block;

-----Architecture Definition
architecture CB_DFLOW of Control_Block is
    signal a, b, cinv: STD_LOGIC;
begin
    cinv <= not Control;
    a <= (Q and Control);
    b <= (Qb and cinv);
    Y <= (a or b);
end CB_DFLOW;
```

Test Bench to test 4 bit Up/Down Asynchronous Counter :

```
-----
-- University:    University of Calcutta
-- Engineer:     Siddhartha Dhar
--
-- Project Name:  Counter_UP_DWN_4b_STRCTL
-----

LIBRARY ieee;
USE ieee.std_logic_1164.ALL;

ENTITY COUNTER_UD_TB IS
END COUNTER_UD_TB;

ARCHITECTURE behavior OF COUNTER_UD_TB IS

    -- Component Declaration for the Unit Under Test (UUT)

    COMPONENT Counter_UD
    PORT(
        CLOCK : IN  std_logic;
        SET   : IN  std_logic;
        CLR   : IN  std_logic;
        CONTROL : IN  std_logic;
        Q : OUT  std_logic_vector(3 downto 0)
    );
    END COMPONENT;

    --Inputs
    signal CLOCK : std_logic := '0';
    signal SET   : std_logic := '0';
    signal CLR   : std_logic := '0';
    signal CONTROL : std_logic := '0';

    --Outputs
    signal Q : std_logic_vector(3 downto 0);

    -- Clock period definitions
    constant CLOCK_period : time := 10 ns;

BEGIN

    -- Instantiate the Unit Under Test (UUT)
    uut: Counter_UD PORT MAP (
        CLOCK => CLOCK,
        SET   => SET,
        CLR   => CLR,
        CONTROL => CONTROL,
        Q => Q
    );

    -- Clock process definitions
    CLOCK_process :process
    begin
        CLOCK <= '0';
        wait for CLOCK_period/2;
        CLOCK <= '1';
        wait for CLOCK_period/2;
    end process;
```

```

-- Stimulus process
stim_proc: process
begin
    -- hold reset state for 100 ns.
    wait for 100 ns;

    wait for CLOCK_period*10;

    -- insert stimulus here
    Control <= '1';
    wait for CLOCK_period*10;
    Control <= '0';
    wait for CLOCK_period*10;
    wait for CLOCK_period*10;
    SET <= '1';
    CLR <= '0';
    wait for CLOCK_period/2;
    SET <= '0';
    CLR <= '0';
    wait for CLOCK_period*10;
    SET <= '0';
    CLR <= '1';
    wait for CLOCK_period/2;
    SET <= '0';
    CLR <= '0';
    wait for CLOCK_period*10;
end process;

END;

```